

GLASGOW COLLEGE UESTC

Final Exam paper

DIGITAL CIRCUIT DESIGN (UESTC3020)

Date: 2 January, 2020

Time: 09:30 – 11:30am

Attempt all PARTS. Total 100 marks

Use one answer sheet for each of the questions in this exam.

Show all work on the answer sheet.

**Make sure that your University of Glasgow and UESTC Student Identification
Numbers are on all answer sheets.**

**An electronic calculator may be used provided that it does not allow text storage
or display, or graphical display.**

**All graphs should be clearly labelled and sufficiently large so that all elements
are easy to read.**

**The numbers in square brackets in the right-hand margin indicate the marks
allotted to the part of the question against which the mark is shown. These
marks are for guidance only.**

Q1 (a) Figure Q1a is an example of a VHDL structural architecture.

```
architecture MY_STRUCT of COMB_LOGIC is
  signal C1, C2: STD_LOGIC;

  component AND port(I0,I1:in STD_LOGIC; O:out STD_LOGIC);
  end component;
  component OR port(I0,I1:in STD_LOGIC; O:out STD_LOGIC);
  end component;
  component NOR port(I0:in STD_LOGIC; O:out STD_LOGIC);
  end component;

begin
  U1: AND port map (A(1), A(0), C1);
  U2: OR port map (A(3), A(2), C2);
  U3: NOR port map (C1, C2, B);
end COMB_LOGIC;
```

Figure Q1a.

- (i) Write down the VHDL entity associated with the architecture of Figure Q1a. [4]
 - (ii) Write down a behavioural VHDL architecture which performs the same function as the structural architecture of figure Q1a. [6]
 - (iii) Explain the main differences between behavioural architecture and structural architecture. [5]
- (b) A simple Field Programmable Gate Array is built from a ‘North-South-East-West’ mesh connected array of Configurable Logic Blocks described in Figure Q1b. We wish to design a circuit which divides the clock frequency by two, and outputs this to the South of the most South-Westerly block of the design.
- (i) Sketch the design of a $\div 2$ circuit using D-type flip-flop. [5]
 - (ii) How many Configurable Logic Blocks are required in total to carry out the logic functions and information routing functions of the $\div 2$ circuit? Give reasons for your answer. [5]

Continued overleaf

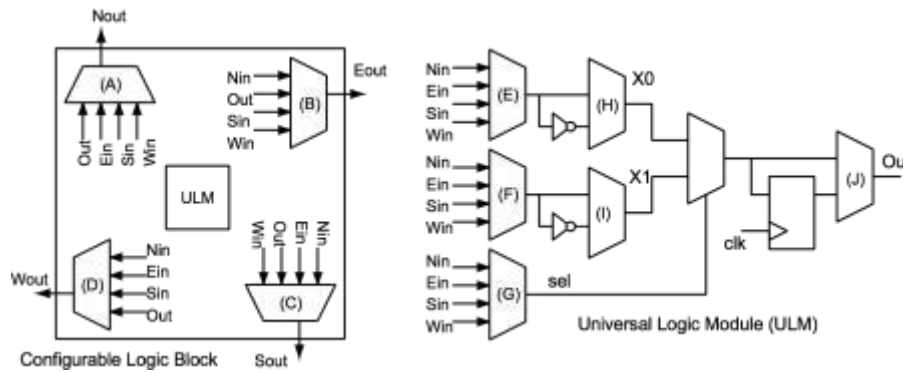


Figure Q1b.

- Q2 (a) A student is required to design a DRAM chip with word size of 4 bits, with row and column address decoders limited to 6 input bits.
- What is the largest memory chip that the student can design under these restrictions? [4]
 - How many decoder NAND gates does the student's design save over one which uses a single large address decoder? [5]
 - What are the advantages and disadvantages of using DRAM compared to using SRAM? [6]
- (b) Memory with read timing parameters described by Figure Q2b is used as part of a synchronous system, with input being fed directly from the outputs of registers with $t_{pd} = 5$ ns (rising clock edge to stable output) and outputs being fed to a register with setup and hold times of $t_s = 3$ ns and $t_h = 2$ ns respectively.
- State the maximum clock frequency at which it can be driven. [7]

 


Figure Q2b.

Continued overleaf

- (c) Describe the benefit of using VHDL in the design of large-scale digital systems. [3]

- Q3 (a) Implement the following Boolean function F , together with the don't-care conditions d , using no more than two NOR gates: [9]

$$F(A, B, C, D) = \sum(2, 4, 10, 12, 14)$$

$$d(A, B, C, D) = \sum(0, 1, 5, 8)$$

Assume that both the normal and complement inputs are available.

- (b) List the eight degenerate two-level forms and show that they reduce to a single operation.
Explain how the degenerate two-level forms can be used to extend the number of inputs to a gate. [16]

- Q4 Design a sequential circuit with two D flip-flops A and B , and one input x_{in}

- (a) When $x_{in} = 0$, the state of the circuit remains the same. When $x_{in} = 1$, the circuit goes through the state transitions from 00 to 01, to 11, to 10, back to 00, and repeats. [13]
- (b) When $x_{in} = 0$, the state of the circuit remains the same. When $x_{in} = 1$, the circuit goes through the state transitions from 00 to 11, to 01, to 10, back to 00, and repeats. [12]

End of question paper