

# **Glasgow College, UESTC**

**Degrees of Bachelor of Engineering (BEng)**

## **MICROELECTRONIC SYSTEMS (UESTC1008)**

**Final Exam**

**5 July 2018**

**10:30 - 12:30**

**Total 4 questions, each of which is worth 25 marks. Total 100 marks.**

**Attempt ALL questions**

*The numbers in square brackets in the right-hand margin indicate the marks allotted to the part of the question against which the mark is shown. These marks are for guidance only.*

**An electronic calculator may be used provided that it does not have a facility for either textual storage or display, or for graphical display.**

## Q1

- a) Convert the following numbers as mentioned. To receive full credit, write the answer and show all your working.

i) Convert 8-bit signed number  $(01011010)_2$  to hexadecimal number. [2]

ii) Convert  $(-26)_{10}$  to signed binary value using 2's complement method. Use 8 bits to represent the result. [3]

- b) With the aid of a circuit diagram, explain how a pull down resistor can be used to reduce the current flow when a switch is connected to the input pin of a microcontroller. [5]

- c) When the code below is compiled to be run on an mbed microcontroller, a number of errors are flagged. Find and correct the errors. [5]

```
#include "mbed.h"
Digital Out myled(LED_1);
int main() {
    while(1) {
        myled = 1;
        pi==3.14;
        wait(0.2);
        myled = 0;
        wait(pi);
    }
}
```

- d) i) What output voltage will be read on a Digital Volt Meter (DVM) connected to pin 18 of an mbed microcontroller when the code below is run on it? [5]

```
#include "mbed.h"
AnalogOut Aout(p18);
int main() {
    for (float i=0;i<1;i=i+0.2){
        Aout=i;
        wait(0.1);
    }
}
```

- ii) When p18 is connected to an oscilloscope, sketch the waveform that is displayed on the oscilloscope? [5]

Continued overleaf

## Q2

(a) Make a circuit diagram (gate level representation) for a 2x4 binary decoder given by the truth table in Figure Q2a. [10]

Truth Table					
A	B	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Fig. Q2a

(b) Figure Q2b represents a 4x1 multiplexer. Provide the corresponding truth table. [10]

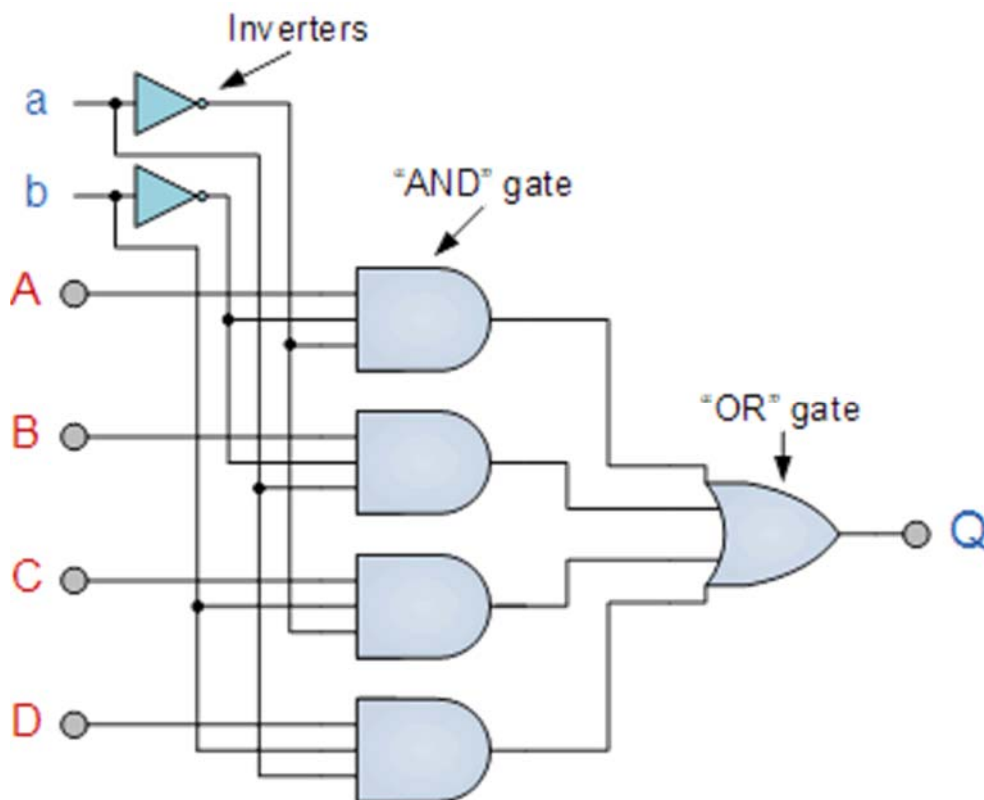


Fig. Q2b

(c) An engineer designed the circuit of Figure Q2c:

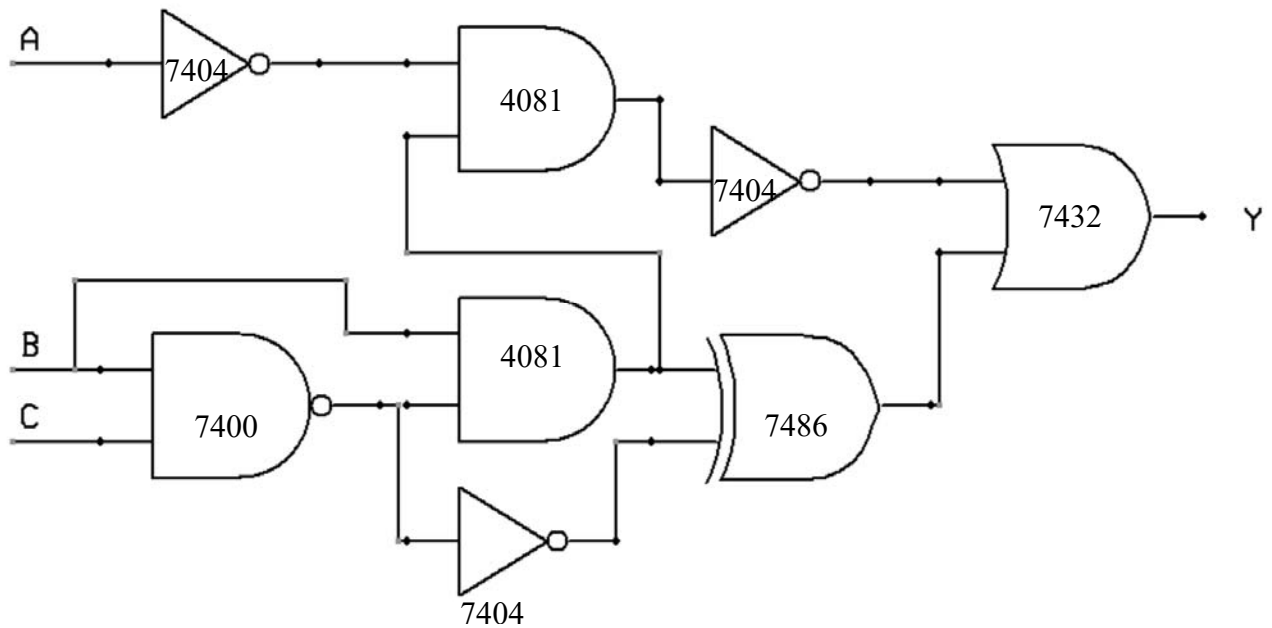


Fig. Q2c

- i) Assuming all the gates in the circuit have equal propagation delay of 10 ms each, what will be the propagation delay of the circuit? [2]
- ii) Which component in the circuit of Figure Q2c can be replaced by the part 7400 configured as shown in Figure Q2d. Hint: Think of the function performed by the component as configured in Figure Q2d. [3]

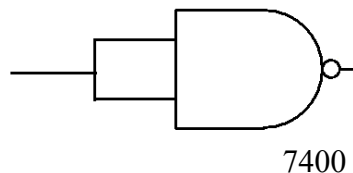


Fig. Q2d

### Q3

(a) Differentiate between Combinational and Sequential logic. Give one example of each type of logic circuit. [5]

(b) Fig. Q3a is a circuit composed of two flip flops. On Fig. Q3b, draw the outputs  $Q_0$  and  $Q_1$  as a function of time, for the given Clock. [10]

#### Assume the following:

The initial state of Q for all the flip-flops is 1.

There is no propagation delay time.

Continued overleaf

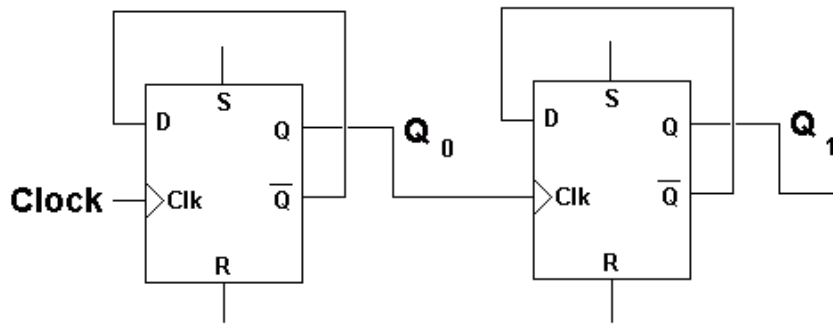


Fig. Q3a

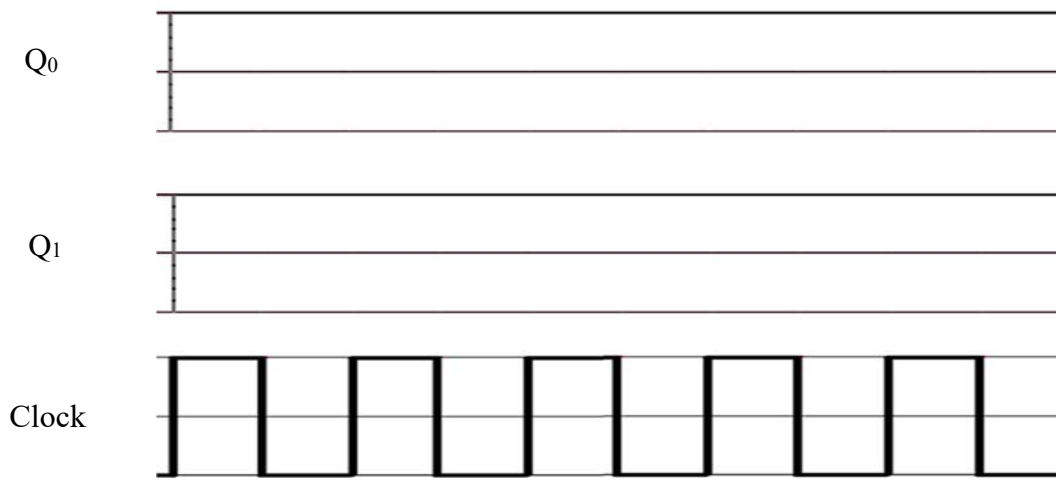


Fig. Q3b

**(b)** For the SR flip flop shown in Fig. Q3c, draw the outputs  $Q$  and  $\bar{Q}$  on Fig. Q3d for given inputs and clock  $C$ .

Assume that the initial state of  $Q$  is 0 and there is no propagation delay time.

[10]

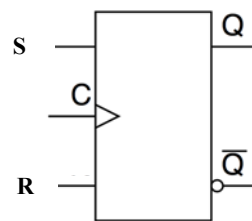


Fig. Q3c

Continued overleaf

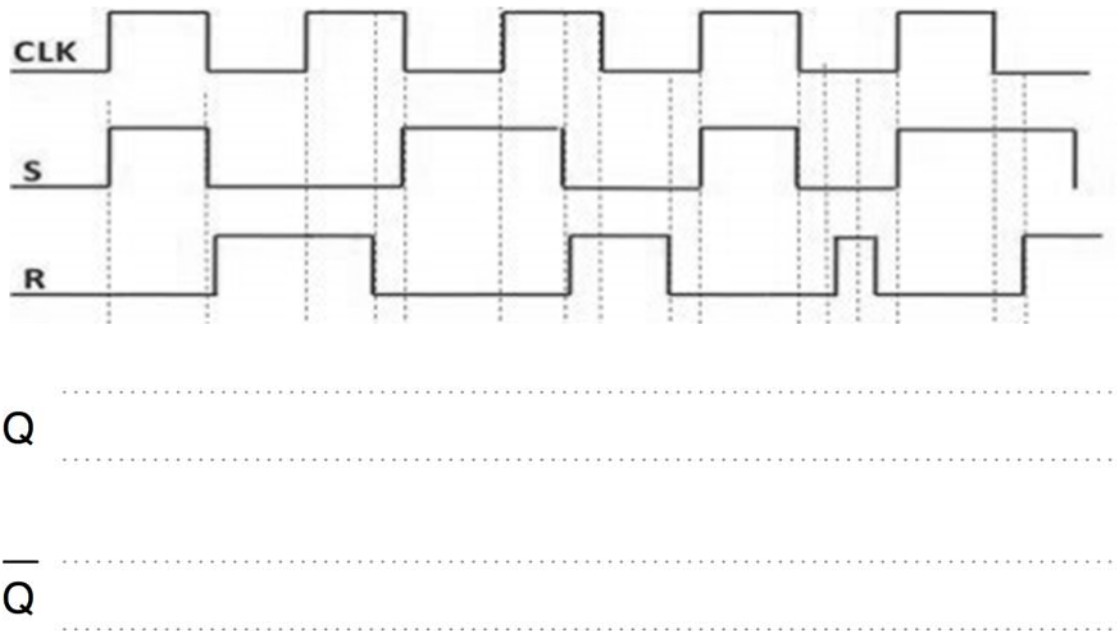


Fig. Q3d

#### Q4

(a) One of the applications of a shift register is a Johnson counter. Shown in Fig. Q4a is a 4 bit shift register made of 4 D type flip flops.

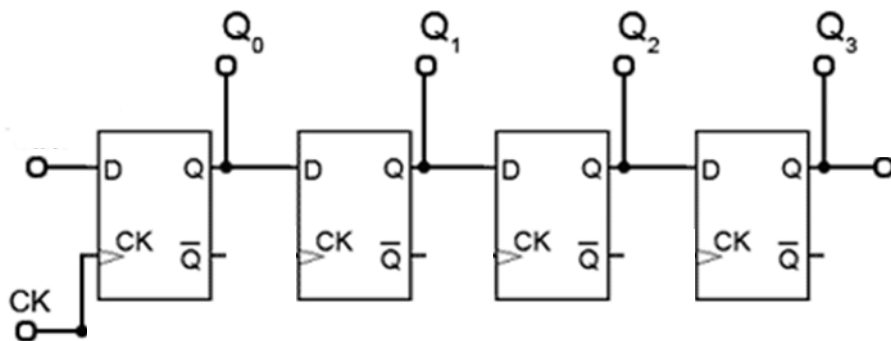


Fig. Q4a

- Redraw the shift register of Fig Q4a to configure it as a Johnson counter. Do not forget to show the direction of data flow and draw the missing connections. [10]
- With reference to a 3 stage counter, explain how a Johnson counter can produce a longer sequence than a Ring counter. Hint: Compare the number of states in a cycle for both counters. [3]
- Write down a truth table showing the different state cycles of a 3 stage Johnson counter. [2]

Continued overleaf

**(b)** An mbed microcontroller is used to produce an analogue signal that is sent to a speaker. The programmer by mistake considers only 7 bits instead of available 10 bits to generate the digital input for the digital to analog converter (DAC).

- i) Given that the reference voltage is 3.3 V, what is the maximum mbed microcontroller analogue output voltage if a 7-bit digital input is used? [3]
- ii) If all 10 bits of the digital input were used, what is the maximum analogue output voltage that could be generated by the mbed microcontroller? [2]
- iii) Calculate the resolution of the 10-bit DAC. [2]
- iv) What would the analogue output voltage be for a digital input 1101010110? [3]

End of question paper