

# **GLASGOW COLLEGE UESTC**

**Exam paper**

## **Communication Circuits Design (UESTC 3029)**

**Date: 26<sup>th</sup> August 2020**

**Time: 14:00-16:00pm**

**Attempt all PARTS. Total 100 marks**

**Use one answer sheet for each of the questions in this exam.**

**Show all work on the answer sheet.**

**Make sure that your University of Glasgow and UESTC Student Identification Numbers are on all answer sheets.**

**An electronic calculator may be used provided that it does not allow text storage or display, or graphical display.**

**All graphs should be clearly labelled and sufficiently large so that all elements are easy to read.**

**The numbers in square brackets in the right-hand margin indicate the marks allotted to the part of the question against which the mark is shown. These marks are for guidance only.**

**DATA/FORMULAE SHEET IS PROVIDED AT THE END OF PAPER**

**Attempt all PARTS**

Continued overleaf

**Q1** A radio system is using a heterodyne AM receiver.

- (a) Sketch a block diagram of the receiver. [4]
- (b) Illustrate waveform shapes at output of each stage for the transmitted message waveform shown in Figure Q4(a). [6]

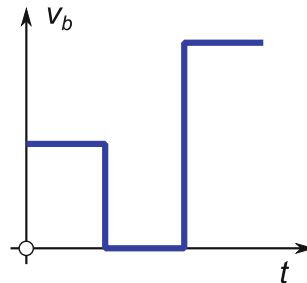


Figure Q4(a)

- (c) This AM receiver is designed to receive RF signals in the 500kHz to 1600kHz frequency range with the required bandwidth of  $B = 10\text{kHz}$  at the resonant frequency  $f_0 = 1050\text{kHz}$ . The RF amplifier uses an inductor of  $L = 1\mu\text{H}$ . Calculate:
- Q factor [2]
  - Bandwidth and capacitance at  $f_{\max} = 1600\text{kHz}$  [6]
  - Bandwidth and capacitance at  $f_{\min} = 500\text{kHz}$  [2]
  - The minimum channel spacing  $\Delta f$  between adjacent AM channels to prevent inter-channel interference. [1]
  - If all incoming RF signals are shifted to intermediate frequency of  $f_{IF} = 465\text{kHz}$  by tuning the receiver through a knob that simultaneously tunes resonating capacitors in the RF amplifier and LO oscillator sections, find the local oscillator's frequency tuneability ratio if  $f_{LO} > f_{RF}$ . [4]

Continued overleaf

- Q2** (a) A radio receiver is tuned to receive an AM signal transmitted at a carrier frequency of  $f_{RF} = 970\text{kHz}$ . The Local Oscillator (LO) inside the receiver is tuned at  $1.43\text{MHz}$ . Find:
- The frequencies at the output of the receiver mixer [4]
  - What frequency is the IF (intermediate filter) frequency [2]
  - The frequency of a radio station that would represent an image frequency to the desired radio station [4]
  - The representative frequency graph (spectrum) of the frequencies involved. [5]
- (b) Consider an ideal single-stage CE amplifier with Miller capacitance caused by additional capacitance present between base and collector ( $C_{CB} = 2\text{pF}$ ) as shown in the figure below, with infinite input resistance and voltage gain of 49 (its absolute value). The amplifier is driven by a voltage source with output resistance  $R_s = 75\Omega$ .

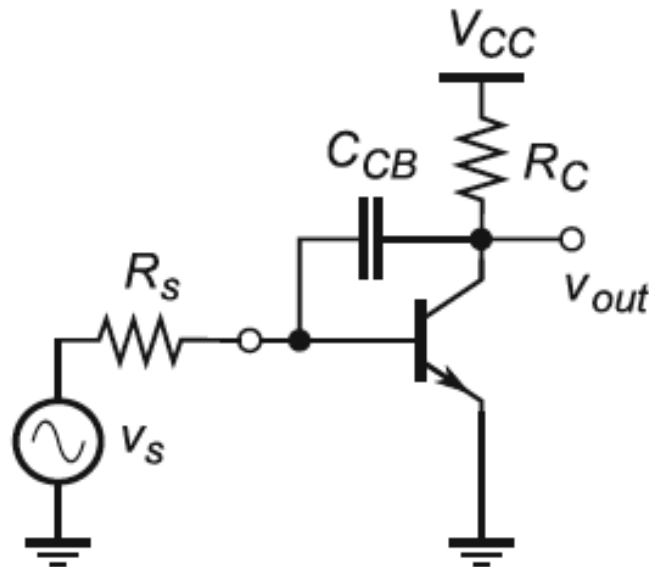


Figure Q2(b)

- Draw the equivalent low pass filter network with miller capacitance. [3]
  - Estimate the useful range of input frequencies for the amplifier with and without considering Miller capacitance effect. [5]
- (c) What is 'near field' of an antenna? [2]

Continued overleaf

- Q3** (a) A tuned radio receiver is to be designed with a single tuned circuit using a  $10\mu\text{H}$  inductor.
- Calculate the capacitance range of the variable capacitor required to tune from 550kHz to 1550kHz. [5]
  - The ideal 10kHz BW is to occur at 1100kHz. Determine the required  $Q$ . [2]
  - Calculate the BW of this receiver at 550kHz and 1550kHz. [4]
- (b) An AM transmitter has a 1kW carrier and is modulated by three different sine waves having equal amplitudes. If  $m_{\text{eff}} = 0.8$ , calculate the individual values of  $m$  and the total transmitted power. [4]
- (c) An unmodulated carrier is 560V<sub>p-p</sub>. Calculate % $m$  when its maximum p-p value reaches 700V. [6]
- (d) Calculate the required  $Q$  for the situation depicted in the Figure 3(d) for the carrier frequency of 100kHz and 80dB sideband suppression. [4]

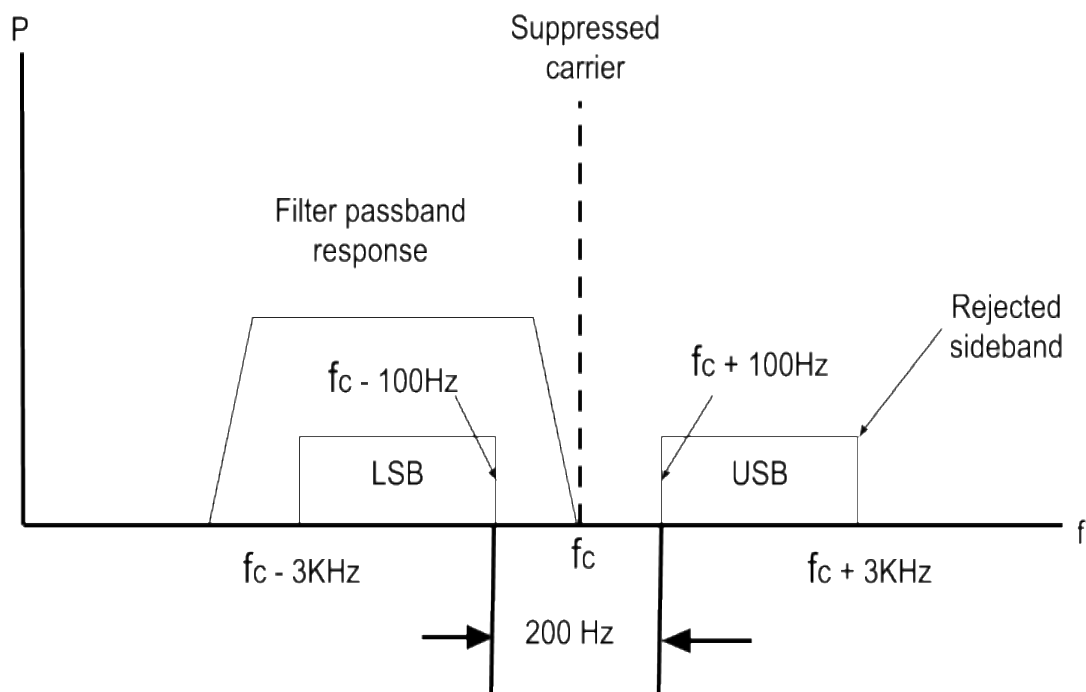


Figure Q3(d)

Continued overleaf

- Q4** (a) Analyse the following communication scenarios and identify the type of communication in terms of simplex, half duplex and duplex. [4]

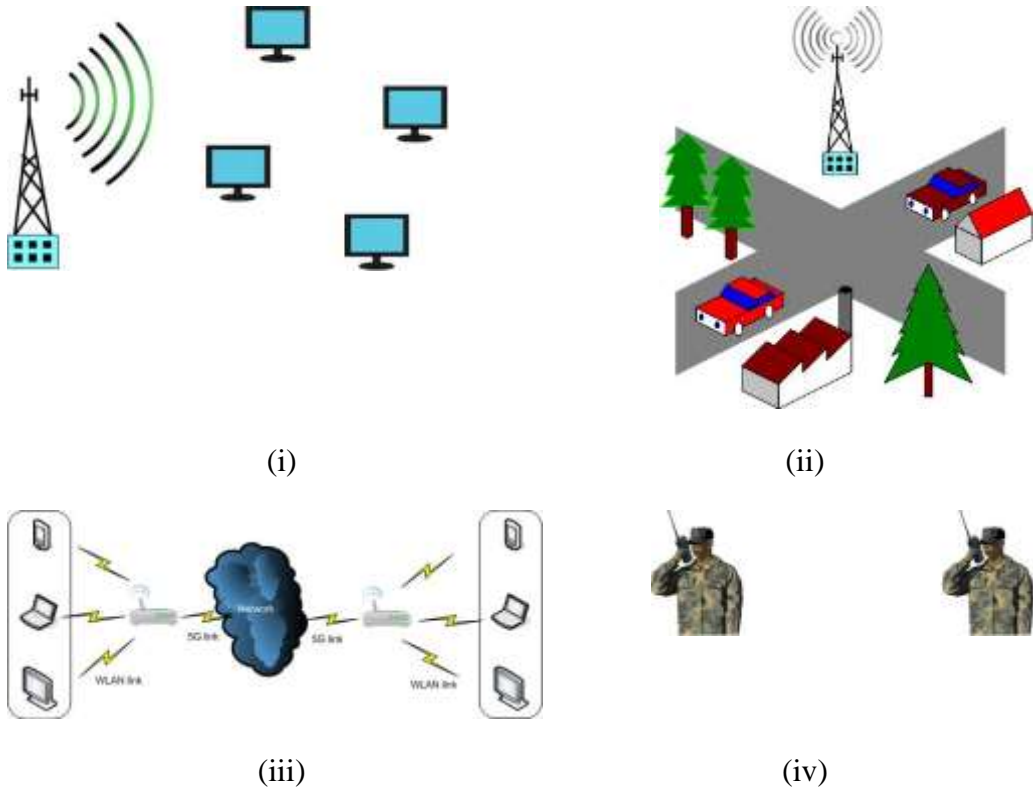


Figure Q4(a)

- (b) The signal power at the input to a receiver is  $6.2\text{nW}$  and the noise power at the input to that receiver is  $1.8\text{nW}$ . Find SNR and  $\text{SNR}_{\text{dB}}$ . [6]
- (c) Multiplexing is an important technique in modern communication systems.
- Define the process of multiplexing. [2]
  - Three radio stations are each allocated a bandwidth of  $8\text{kHz}$  respectively. They broadcast radio waves into free space at carrier frequencies of  $80$ ,  $90$  and  $100\text{kHz}$  respectively. The guard band between each channel is  $2\text{kHz}$ . Determine the type of multiplexing. [1]
  - Find frequency allocation (band) for each station given in Part (ii) and represent this information on a frequency spectrum graph. [3]
  - Represent the frequency allocation information of Part (iii) on a frequency spectrum graph. [3]

Continued overleaf

- (d) The receiver of a communication system uses the amplifier circuit of Figure Q4(d). Determine the values of  $V_{DS}$  and  $V_{GS}$ . [6]

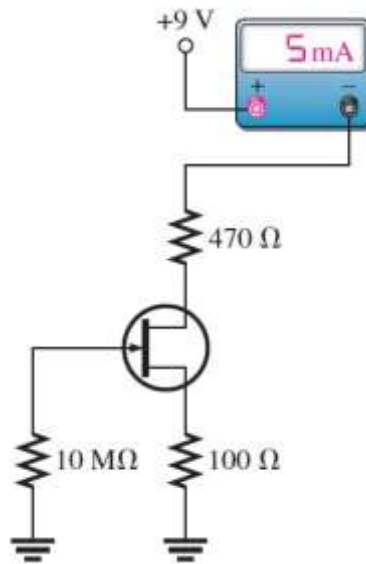


Figure Q4(d)

## FORMULAE SHEET

$$|A_r| = \frac{|V_0|}{V_0(\omega_0)} = \frac{1}{\sqrt{1+(\delta Q)^2}} \quad \delta = \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}$$

$$RL = -20 \log_{10} \left| \frac{V_{ref}}{V_{inc}} \right|; \quad VSWR = \frac{1+10^{-\frac{RL}{20}}}{1-10^{-\frac{RL}{20}}}$$

$$Q_L = \frac{\text{reactance}}{\text{resistance}} = \frac{\omega L}{R}; \quad Q_C = \frac{\text{susceptance}}{\text{conductance}} = \frac{\omega C}{G} = \omega CR; \quad Q = \frac{f_0}{BW}$$

$$R_P = R_S(1 + Q^2); \quad X_P = X_S(1 + \frac{1}{Q^2})$$

$$C_D = C_{Varactor} \approx \frac{C_0}{\sqrt{1+\frac{|V_D|}{0.5}}} \quad C_{Miller} = C(A_v + 1)$$

	Input R <sub>i</sub>		Output R <sub>o</sub>		Gain A <sub>v</sub>
	Large R <sub>L</sub>	Small R <sub>L</sub>	Large R <sub>S</sub>	Small R <sub>S</sub>	
<b>CB</b>	R <sub>E</sub> +R <sub>B</sub>	R <sub>E</sub>	R <sub>C</sub> +R <sub>b</sub>	R <sub>C</sub> $\frac{R_e + R_b(1-\alpha)}{R_e + R_b}$	$\frac{R_L}{R_S + R_i}$
<b>CE</b>	r <sub>i</sub> = r <sub>b</sub> + r <sub>e</sub> ≈ r <sub>b</sub>	r <sub>b</sub> + β r <sub>e</sub>	r <sub>e</sub> + $\frac{r_c}{\beta}$	r <sub>c</sub> $\frac{r_e + \frac{r_b}{\beta}}{r_b + r_e} \approx r_c$	$\frac{R_C}{R_b + R_e}$
<b>CC</b>	r <sub>i</sub> = r <sub>b</sub> + r <sub>e</sub> ≈ r <sub>c</sub>	r <sub>b</sub> + $\frac{r_c}{1-\alpha} = r_b + \beta r_e$	r <sub>b</sub> + r <sub>c</sub> (1-α) ≈ $\frac{r_c}{\beta}$	r <sub>e</sub> + $\frac{r_b}{\beta} \approx r_e \approx \frac{1}{g_m}$	$\frac{R_L}{R_L + R_S/\beta}$

$$B_{-1dB} = \sqrt{0.145 \left| \frac{a_1}{a_3} \right|}; \quad B_{IIP3} = \sqrt{4/3 \left| \frac{a_1}{a_3} \right|}; \quad B_{-1dB} = IIP3 - 9.6dB$$

$$DR = 1dB_{point} - S_n; \quad S_n = P_n + SNR; \quad P_{n,input} = 10 \log_{10}(kT \Delta f_{eff})$$

$$k = 1.38 \times 10^{-23}$$

End of question paper