

GLASGOW COLLEGE UESTC

Exam paper

Microelectronic Systems (UESTC1008)

Date: 24th June 2019

Time: 14:30-16:30pm

Attempt all PARTS. Total 100 marks

**Use one answer sheet for each of the questions in this exam.
Show all work on the answer sheet.**

**Make sure that your University of Glasgow and UESTC Student Identification
Numbers are on all answer sheets.**

**An electronic calculator may be used provided that it does not allow text storage
or display, or graphical display.**

**All graphs should be clearly labelled and sufficiently large so that all elements
are easy to read.**

**The numbers in square brackets in the right-hand margin indicate the marks
allotted to the part of the question against which the mark is shown. These
marks are for guidance only.**

DATA/FORMULAE SHEET IS PROVIDED AT THE END OF PAPER

Q1 (a) The below code will generate a waveform

```
1. #include "mbed.h"
2. PwmOut led(LED1);
3. int main() {
4.     led.period(4.0f);
5.     led.write(0.50f);
6.     while(1);
7. }
```

- (i) What will be the duty cycle of this waveform? [2 marks]
- (ii) Draw the shape of the waveform that will be output by the mbed by properly labelling the time period of the waveform? [3 marks]
- (iii) Explain the purpose of each line in the code. [10 marks]

(b) Memory architectures:

- (i) What are the two different type of memory architectures used in microcomputers [2 marks]
- (ii) Sketch a diagram of each of the two memory architectures [5 marks]
- (iii) Explain the difference between the two memory architectures [3 Marks]

Q2 (a) A green LED, which drops 2.1 V when current is flowing through it, is connected to the DigitalOut pin of a mbed microcontroller. The battery life of the system is to be increased by limiting the current flowing through the LED to 2mA using a series connected resistor. For an mbed with 3.6 V output voltage, what value of series resistor is required? [5 marks]

(b) Determine the truth table for the circuit configuration shown in Fig Q2b in which MA and MB are NMOS switches connected to input A and B respectively while ML is

Continued overleaf

working as load transistor. The truth table should have inputs A & B and output Vo.

[10 marks]

 


Fig Q2b

(c) A bit sequence 010111010011 is given at the input of a 3-bit Digital to Analog Converter (DAC) whose reference voltage V_r is 3.3 V.

- (i) Calculate the analog output voltage V_o for input 111. [2 marks]
- (ii) Assuming one DAC conversion takes $2\mu s$. How long will it take to convert the whole bit sequence? [3 marks]
- (iii) For a controller with 40 MHz clock speed, how many clock cycles would be required for the whole conversion? [5 marks]

Q3 (a) For the Boolean function

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$

- (i) Draw the truth table of F. [5 marks]
- (ii) Draw the logic diagram using the original Boolean expression. [5 marks]

Continued overleaf

- (b) Write a Boolean expression and construct the truth table for the logic diagram of Fig Q3b: [10 marks]

 


Fig Q3b

- (c) Using block diagrams, sketch a 16x1 multiplexer which is created from two 8x1 and one 2x1 multiplexers. [5 marks]

Q4 (a) What is the difference between a sequential logic and a combinational logic circuit? [5 marks]

(b) Why are clocks used in latches? [5 marks]

- (c) Redraw Fig Q4c2 below and add the outputs Q1, Q2 and Q3 from the circuit of Fig Q4c1. Assume the circuit clock operates at the rising edge and that all Q outputs are initialized as 1. [15 marks]

 


Fig Q4c1

Continued overleaf

 


Fig Q4c2